

DLD
Mid semester Exam
IITS, Chittoor

Date: 25/03/2022

Duration: 90 Mins

Maximum Marks: 25M

Instructions


- a) Answer all questions
 - b) Do not copy from any source, if found, you will be penalized according to institute norms.
 - c) Write neatly in A4 sheets (White).
 - d) On all pages write
 - a. Your name
 - b. Roll number
 - c. Question paper code
 - e) Scan properly and convert into.pdf format as a single file (Only pdf is allowed)
 - f) **For uploading the file in Google form, Name the file as "Rollno.pdf"**
If you don't upload the correct file or if you submit an invalid file, e-mailing faculty or uploading later is not allowed.
-

Paper Code B


1. Implement the following Boolean expression using 2:4 Decoder and other external logic gates.

$$F(A, B, C) = AC + A'BC + B'C'$$

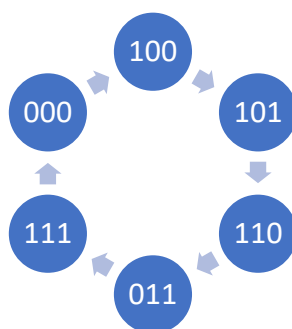2. Design a magnitude comparator circuit to compare the following inputs. A= 111; B= 010
3. Design the counter using D flip-flop which the following state diagram



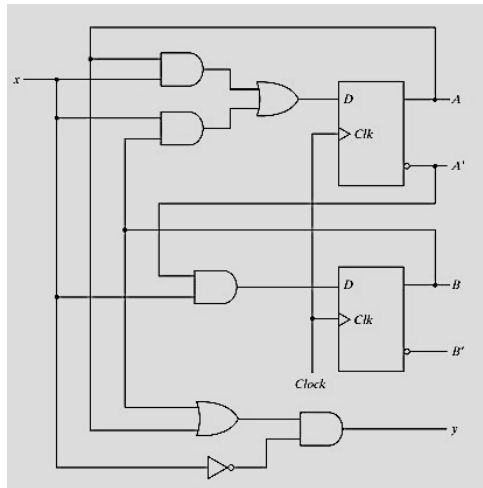4. Determine the Next State and Output value of the following circuit, when the present state of the $A(t)=0$, $B(t)=1$, and input $x(t)=1$.



5. Draw a 2 x 2 RAM circuit. Write Verilog code for the following circuit.

